



1. Live to T1
2. Negative to T3
3. Sensor P1 to STC 3
4. Sensor P2 to STC 4
5. Thermostatic switch SW1 to T1
6. Thermostatic switch SW2 to T2
7. Fan F1 to T3
8. Fan F2 to T2
9. STC 1 to T2
10. STC 2 to T3
11. STC 5 to T2
12. STC 6 to T4
13. Feed the bulb wires into the Junction box
14. Feed to probe out of the Junction box.
15. Bulb B1 to T4
16. Bulb B2 to T3
17. Connect the power and test

This wiring diagram relates to the following video : <https://youtu.be/2yfPKFgvmes>